

CE303 HW#3

P3: To get from inputs A_0, B_0, C_0 to S_3 we use 2 XOR per ^{by the critical path} ^{in series}

a) adder, meaning ~~2x4x3~~ $2 \times 4 \times 3 = 24$ time units

To get from inputs A_0, B_0, C_0 to C_4 we use 2 XOR per ^{by the critical path} ^{in series} adder for the first 3 adders & then 1 AND & 1 OR, meaning $2 \times 3 \times 3 + 2 = 20$ time units

b) Given - Sum delay is 2 times Carry delay:

↳ worst case goes through 20 FA, 13 carries & 7 sums

↳ $D_s = 2, D_c = 1 \rightarrow 13 \times 7 \times 2 = 27$


Given Carry delay is 2 times Sum delay:

↳ worst case goes through 20 FA, 14 carries & 6 sums

↳ $D_s = 1, D_c = 2 \rightarrow 14 \times 2 + 6 = 34$

↳ I would favor having faster carries

P4:

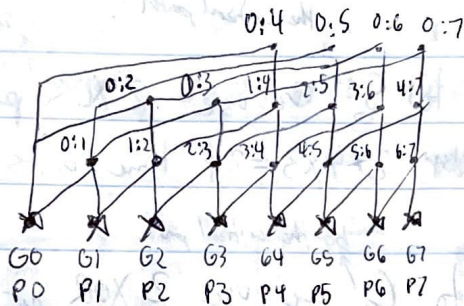

The ~~critical~~ critical path involves 3 dot products, ~~and~~ at each dot product the critical path goes through 1 AND gate and 1 OR gate and at the beginning G_0 & P_0 are created ~~from~~ by a single gate each in parallel $\rightarrow 3 \times 2 + 1 = 7$ gates

\hookrightarrow Critical Path: ~~AB = G~~ ~~AB = G~~ ~~AB = G~~ ~~AB = G~~ ~~AB = G~~ ~~AB = G~~ ~~AB = G~~ ~~AB = G~~

$$\begin{array}{ccccccc} \text{1st gate} & & \text{2nd gate} & & \text{3rd gate} & & \text{4th gate} \\ A_0 B_0 = G_0 & \rightarrow & P_0 G_0 + G_0 & = & G_0 & \rightarrow & P_0 G_0 + G_0 = G_0 \\ & & & & 0:1 & & 2:3 \quad 0:1 \quad 2:3 \quad 0:3 \\ & & & & & & 4th \quad 5th \\ & & & & & & \text{gate} \quad \text{gate} \end{array}$$

$$\begin{array}{ccccccc} \text{6th gate} & & \text{7th gate} \\ G_0 & \rightarrow & P_0 G_0 + G_0 & = & G_0 & \rightarrow & P_0 G_0 + G_0 = G_0 \\ & & 0:3 & & 4:7 \quad 0:3 & & 4:7 \quad 0:7 \end{array}$$